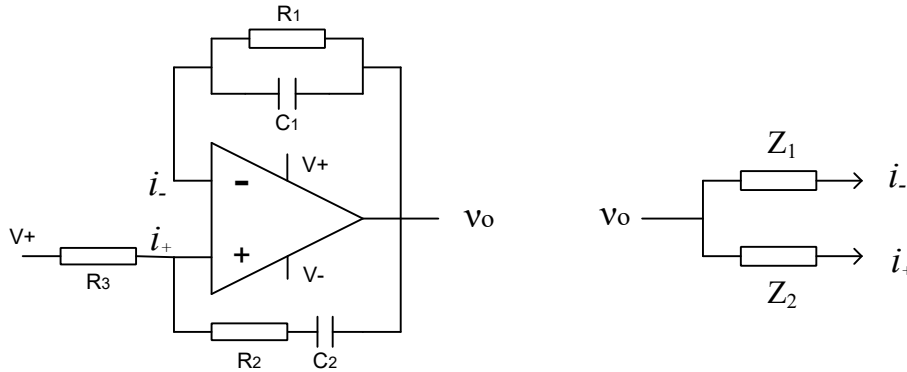


# Analysis of Sinewave Circuits

Mauri Lampi - [soliton@optusnet.com.au](mailto:soliton@optusnet.com.au)

Three sinewave oscillator circuits based on Norton operational amplifier are analysed here using mesh current method. Mathematics of Circuit 1 is quite simple, involving only two currents. Circuits 2 and 3 have an extra loop current. See reference at the end of this document.

## Circuit 1



$R_3$  is a bias resistor.  $R_3 = 2 \cdot R_1$  therefore dc value of  $|v_o| = \frac{1}{2} V_+$

### Circuit analysis:

This simplified analysis of Circuit 1 allows one to select circuit elements to meet the condition for oscillation and determine the resulting frequency of oscillation.

$$Z_1 = \frac{\frac{R_1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1}{j\omega R_1 C_1 + 1}$$

$$Z_2 = R_2 + \frac{1}{j\omega C_2}$$

For sustained oscillation:

$$i_+ = i_- \text{ therefore } Z_1 = Z_2$$

$$\frac{R_1}{j\omega R_1 C_1 + 1} = R_2 + \frac{1}{j\omega C_2}$$

$$\frac{j\omega R_1 C_2}{j\omega R_1 C_1 + 1} = j\omega R_2 C_2 + 1$$

$$j\omega R_1 C_2 = -\omega^2 R_1 C_1 R_2 C_2 + j\omega R_1 C_1 + j\omega R_2 C_2 + 1$$

Equate real and imaginary parts:

**REAL** (gives frequency of oscillation):

$$\omega^2 R_1 C_1 R_2 C_2 = 1$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\omega = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}} \text{ r/s}$$



$$f = \frac{\omega}{2\pi} \text{ Hertz}$$

**IMAGINARY** (gives the condition for oscillation):

$$j\omega R_1 C_2 = j\omega R_1 C_1 + j\omega R_2 C_2$$

$$R_1 C_2 = R_1 C_1 + R_2 C_2 = 1$$
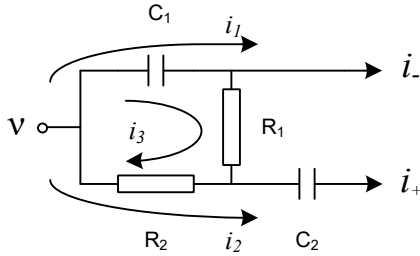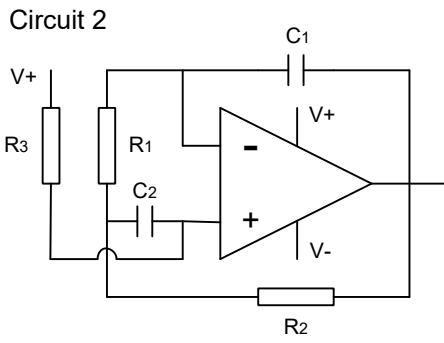
$$\frac{R_2}{R_1} + \frac{C_1}{C_2} = 1$$



Mesh currents

Circuit 2: Impedance matrix

$$\Delta Z = \begin{vmatrix} \frac{1}{sC_1} & 0 & \frac{1}{sC_1} \\ 0 & R_2 + \frac{1}{sC_2} & -R_2 \\ \frac{1}{sC_1} & -R_2 & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix}$$

$$\Delta Z \cdot \mathbf{i}_1 = \begin{vmatrix} v & 0 & \frac{1}{sC_1} \\ v & R_2 + \frac{1}{sC_2} & -R_2 \\ 0 & -R_2 & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix}$$

$$(\Delta Z \cdot \mathbf{i}_1) / v = \Delta_{11} + \Delta_{21}$$

$$= \begin{vmatrix} R_2 + \frac{1}{sC_2} & -R_2 \\ -R_2 & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix} - \begin{vmatrix} 0 & \frac{1}{sC_1} \\ -R_2 & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix}$$

$$\begin{aligned}
&= R_1 R_2 + R_2^2 + \frac{R_2}{sC_1} + \frac{R_1}{sC_2} + \frac{R_2}{sC_2} + \frac{1}{s^2 C_1 C_2} - R_2^2 - \frac{R_2}{sC_1} \\
&= R_1 R_2 + \frac{R_1}{sC_2} + \frac{R_2}{sC_2} + \frac{1}{s^2 C_1 C_2}
\end{aligned}$$

$$\Delta Z \cdot i_2 = \begin{vmatrix} \frac{1}{sC_1} & v & \frac{1}{sC_1} \\ 0 & v & -R_2 \\ \frac{1}{sC_1} & 0 & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix}$$

$$(\Delta Z \cdot i_2) / v = \Delta_{12} + \Delta_{22}$$

$$\begin{aligned}
&= \begin{vmatrix} 0 & -R_2 \\ \frac{1}{sC_1} & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix} - \begin{vmatrix} \frac{1}{sC_1} & \frac{1}{sC_1} \\ \frac{1}{sC_1} & R_1 + R_2 + \frac{1}{sC_1} \end{vmatrix} \\
&= -\frac{R_2}{sC_1} + \frac{R_1}{sC_1} + \frac{R_2}{sC_1} + \frac{1}{s^2 C_1^2} - \frac{1}{s^2 C_1^2} \\
&= \frac{R_1}{sC_1}
\end{aligned}$$

For sinusoidal signal:

$$s^2 = (j\omega)^2 = -\omega^2$$

$$\frac{1}{s^2 C_1 C_2} = -\frac{1}{\omega^2 C_1 C_2}$$

For stable sinusoidal oscillation

$$i_1 = i_2$$

Therefore:

$$[(\Delta Z \cdot i_1) / v] = [(\Delta Z \cdot i_2) / v]$$

Equating real and imaginary parts of  $i_1$  and  $i_2$ :

**Real** (gives the frequency of oscillation):

$$R_1 R_2 - \frac{1}{\omega^2 C_1 C_2} = 0$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\omega = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}} \text{ r/s}$$


$$f = \frac{\omega}{2\pi} \text{ Hertz}$$

**Imaginary** (gives the condition for oscillation)


$$\frac{R_1}{C_2} + \frac{R_2}{C_2} = \frac{R_1}{C_1}$$

$$\frac{C_2}{C_1} = 1 + \frac{R_2}{R_1}$$

Circuit 3

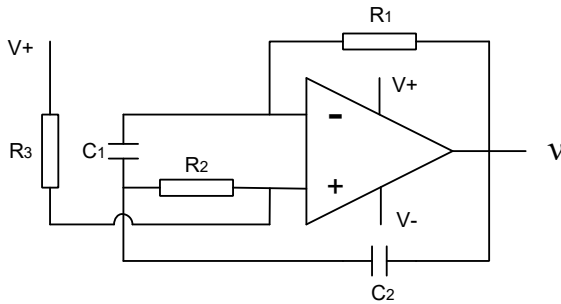

Circuit 3 Mesh currents

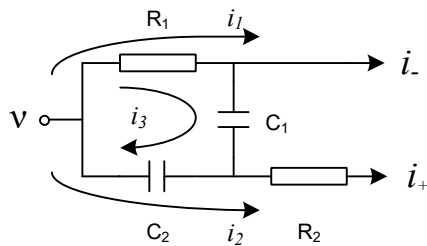

Circuit 3: Impedance matrix

$$\Delta Z = \begin{vmatrix} R_1 & 0 & R_1 \\ 0 & R_2 + \frac{1}{sC_1} & -\frac{1}{sC_2} \\ R_1 & -\frac{1}{sC_2} & R_1 + \frac{1}{sC_1} + \frac{1}{sC_2} \end{vmatrix}$$

$$\Delta Z \cdot \mathbf{i}_1 = \begin{vmatrix} v & 0 & R_1 \\ v & R_2 + \frac{1}{sC_2} & -\frac{1}{sC_2} \\ 0 & -\frac{1}{sC_2} & R_1 + \frac{1}{sC_1 C_2} \end{vmatrix}$$

$$(\Delta Z \cdot \mathbf{i}_1) / v = \Delta_{11} + \Delta_{21}$$

$$\begin{aligned} &= \begin{vmatrix} R_2 + \frac{1}{sC_2} & -\frac{1}{sC_2} \\ -\frac{1}{sC_2} & R_1 + \frac{1}{sC_1} + \frac{1}{sC_2} \end{vmatrix} - \begin{vmatrix} 0 & R_1 \\ -\frac{1}{sC_2} & R_1 + \frac{1}{sC_1} + \frac{1}{sC_2} \end{vmatrix} \\ &= R_1 R_2 + \frac{R_2}{sC_1} + \frac{R_2}{sC_2} + \frac{R_1}{sC_2} + \frac{1}{s^2 C_1 C_2} - \frac{1}{s^2 C_2^2} - \frac{R1}{sC_2} \\ &= R_1 R_2 + \frac{R_2}{sC_1} + \frac{R_2}{sC_2} + \frac{1}{s^2 C_1 C_2} \end{aligned}$$

$$\begin{aligned}
(\Delta z \cdot i_2) / \mathcal{V} &= \Delta_{12} + \Delta_{22} \\
&= \begin{vmatrix} 0 & -\frac{1}{sC_2} \\ R_1 - \frac{1}{sC_2} & R_1 + \frac{1}{sC_1} + \frac{1}{sC_2} \end{vmatrix} - \begin{vmatrix} R_1 & R_1 \\ R_1 & R_1 + \frac{1}{sC_1} + \frac{1}{sC_2} \end{vmatrix} \\
&= -\frac{R_1}{sC_2} + R_1^2 + \frac{R_1}{sC_1} + \frac{R_1}{sC_2} - R_1^2 \\
&= \frac{R_1}{sC_1}
\end{aligned}$$

For sinusoidal signal:

$$\begin{aligned}
s^2 &= (j\omega)^2 = -\omega^2 \\
\frac{1}{s^2 C_1 C_2} &= -\frac{1}{\omega^2 C_1 C_2}
\end{aligned}$$

For stable sinusoidal oscillation

$$i_1 = i_2$$

Therefore:

$$[(\Delta z \cdot i_1) / \mathcal{V}] = [(\Delta z \cdot i_2) / \mathcal{V}]$$

Equating real and imaginary parts:

**Real** (gives the frequency of oscillation):

$$R_1 R_2 - \frac{1}{\omega^2 C_1 C_2} = 0$$

$$R_1 R_2 = \frac{1}{\omega^2 C_1 C_2}$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\omega = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}} \text{ r/s}$$

$$f = \frac{\omega}{2\pi} \text{ Hertz}$$

**Imaginary** (gives the condition for oscillation)

$$\frac{R_1}{C_1} = \frac{R_2}{C_1} + \frac{R_2}{C_2}$$

$$\frac{R_1}{R_2} = 1 + \frac{C_1}{C_2}$$

*Reference:* Schaum's Outline Series  
ELECTRIC CIRCUITS  
By Joseph A. Edminister